

Mid-West University
Examinations Management Office

End Semester Examinations 2081

Bachelor level/ B.E. Hydropower/ 3rd Semester

Full Marks: 50


Time: 3 hours

Pass Marks: 25


Subject: Basic Electronics Engineering (EX201)

- Attempt all the questions
- Figures in the margin indicate full marks.
- Assume suitable values, with a stipulation, if necessary.
- Candidates are required to answer the questions in their own words as far as possible.

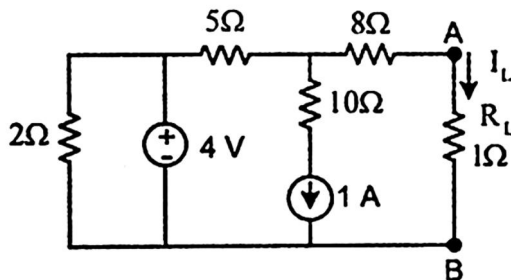
1. a. Define active and passive components. Find the value of resistance of color **Black Orange Green Silver**. [2+2]
- b. Determine the current through the load resistance using Norton's theorem for the circuit shown in Figure. [4]



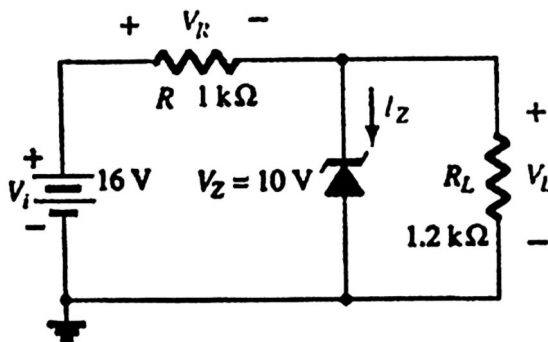2. a. Explain Clamper and Clippers diode circuit with necessary circuit diagram? [3]
- b. Calculate current and power delivered by Zener diode. [4]



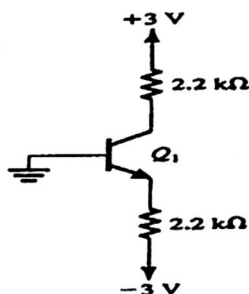3. a. Explain the structure and operation of Depletion N-type MOSFET. [3]
- b. For the circuit given below calculate all node voltages and branch currents. [4]



4. a. Explain inverting and non-inverting Op-Amp. Calculate the output voltage of operational amplifier differentiator circuit [2+3]
- b. Calculate the oscillation frequency of square wave generator. [2]

5. a. Define antenna and list out its types. [2]
b. Explain FM and AM communication. [3]
6. a. State and proof De Morgan's theorem, Design (8X1) MUX circuit. [2+3]
b. What is sequential circuit. Explain the operation of SR flip-flop. [3]
c. Simplify the Boolean function by using K-map $F(x, y, z) = \sum(1,2,4,6,7)$. [2]
7. a. Define remote control with their applications. [3]
b. Write the difference between analog and digital instrumentation system. [3]

The End