

Mid-West University
Examinations Management Office
End-Semester Examinations -2080

Bachelor level / B.E. Computer / 2nd Semester

Time: 3 hours

Subject: Logic Circuits (EX421/EX501)

Full Marks: 50

Pass Marks: 25

- Attempt all the questions
- Figures in the margin indicate full marks.
- Assume suitable values, with a stipulation, if necessary.
- Candidates are required to answer the questions in their own words as far as possible.

1. Perform the following operation: 1x5
 - i) $(76526.543)_8 = (?)_{16}$
 - ii) $(89744.012)_{10} = (?)_8$
 - iii) $(10111001001.100101)_2 = (?)_{10}$
 - iv) Convert $(11011011)_2$ to Gray code
 - v) Find the 2's complement of $(101110110110)_2$
2. Why NAND and NOR gates are called universal gates? Explain your answer. 4
3. Simplify the following Boolean function using K- map in a i) Product of sum and ii) Sum of products and implement it with logic gates: 3+3
 $F(W,X,Y,Z) = \sum (0,1,3,6,8,12,14)$ and don't care conditions: $d(W,X,Y,Z) = \sum (4,5,10,13)$.
4. Explain magnitude comparator with necessary circuit diagram. 4
5. Divide $(1011101)_2$ by $(101)_2$ using repeated subtract and left shift algorithm. 4
6. Explain about the switch contacts bound circuits with necessary diagram. 4
7. Explain SIPO register with its timing diagram. 3
8. Explain about 3-bit ripple up counter with timing diagram. 5
9. a. A synchronous machine has one-bit serial input A and the output B of the machine is to be set high when the input contains the message '011'. Draw the state diagram, derive state table and design the circuit diagram. 6
b. Explain about the Critical race in sequential machine 2
10. Differentiate between TTL and CMOS. Briefly explain TTL-to-CMOS interface. 3+2
11. Explain briefly about the Frequency counters. 2

The End