


Mid-West University
Examinations Management Office
End-Semester Examinations -2080

Bachelor level/ B.E. Hydropower/ II Semester
Time: **3** hours
Subject: **Basic Electronics Engineering (EX421)**

Full Marks: 50
Pass Marks: 25

- Attempt all the questions
- Figures in the margin indicate full marks.
- Assume suitable values, with a stipulation, if necessary.
- Candidates are required to answer the questions in their own words as far as possible.

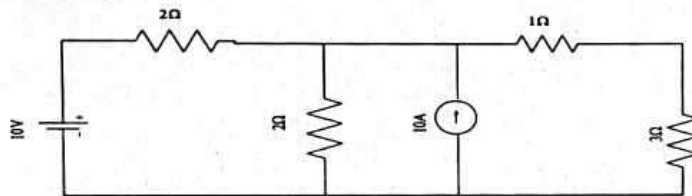1. a) Explain linear and non-linear circuits. 2
- b) Determine the current through 3Ω resistor in the circuit given below using Thevenin's Theorem: 4



2. a) Explain varactor diode and zener diode in detail 2+2
- b) A Si diode has the saturation current of 0.3 pA at 25°C . Find its current when it is forward biased by 0.5 V . Find the current in the same diode when the temperature rises to 95°C . 4
3. a) Explain about CB biasing of the BJT. 4
- b) Find the value of collector current, Q point and DC load line for common emitter circuit having $V_{cc} = 15\text{V}$, $R_c = 10\text{K}\Omega$, $I_B = 10\mu\text{A}$ and $\beta = 50$. 4
4. a) Explain about the subtractor circuit using Op-amp with necessary expression. 4
- b) Explain in detail about the generation of triangular wave using op-amp. 4
5. a) Explain about the digital communication system and write its advantages over analog communication system. 2+1
- b) What is modulation? Why it is necessary? 1+2
6. a) Explain about the types of basic logic gates with truth tables. 3
- b) What is encoder? Explain it with necessary circuit diagram. 3
- c) Simplify the following expression in POS form using k-map and draw the circuit diagram. $F(W,X,Y,Z) = \sum(0,1,3,5,6,12,13,14)$ 4
7. What is transducer? Explain its type. 1+3

The End